Monolithic Linear IC

	No.1595B	LA5655
SANYO		Voltage Regulator for FLT Display Desk-Top Calculator

The LA5655 is an IC containing all the voltage regulators required for an FLT display desk-top calculator with a printer.

Features and Functions

- a. On-chip voltage regulators required for desk-top calculator (FLT display) with a printer.
 - 1. Printer voltage regulator.
 - 2. LSI voltage regulator.
 - 3. FLT anode, grid voltage regulator.
 - 4. FLT heater grid voltage regulator.
 - 5. FLT bias grid voltage regulator.

b. On-chip printer motor brake circuit

Maximum Ratings at Ta=25°C			unit
Voltage Regulator Input Voltage 1	V _{TN1}	50	V
Voltage Regulator Input Voltage 2	VTN2	25	V
Output Current 1	I _{OUT1}	40	mA
Output Current 2	I _{OUT2}	2.0	A
Output Current 3	IOUTX	(X=3,4,5) other regulator 40	mA
Allowable Power Dissipation	Pdmax	IC alone 2.45	W
Operating Temperature	Topr	-20 to +75	°c
Storage Temperature	Tstg	-40 to +125	°C
Operating Conditions at Ta=25 ⁰ C			unit
Voltage Regulator	V _{IN1}	+20 to +50	V
Input Voltage Range			
MT Pin H Voltage	VENAH	2.0 to 7.0	v
MT Pin L Voltage	VENAL	-0.3 to +0.3	v



SANYO Electric Co., Ltd. Semiconductor Business Headquarters TOKYO OFFICE Tokyo Bldg., 1-10, 1 Chome, Ueno, Taito-ku, TOKYO, 110 JAPAN

LA!	565	5
-----	-----	---

Operating Characteristics a	at Ta=25 ⁰ C V	IN1=35V, V _{IN2} =10V, I _{OU}	T2=200)mA		
Out and Wells			min	typ	max	unit
Output Voltage 1	VOUT1	①→⑧ I _{OUT1} =30mA	28.5	30	32.5	V
Output Votlage 2	V _{OUT2}	(7)→(8)	5.3	5.6	6.0	V
Output Voltage 3	V _{OUT3}		13.8	15	16.2	v
Output Votlage 4	V _{OUT4}		4.6		5.4	V
Output Votlage 5	V _{QUT5}	3-8 IIN5=30mA	7.3	8	8.7	v
Load Regulation 1	^{∆V} 01LOAD	10mA <iout1<30ma< td=""><td></td><td></td><td>250</td><td>mÅ</td></iout1<30ma<>			250	mÅ
Load Regulation 2	△V02LOAD	100mA <iout2<2a< td=""><td></td><td></td><td>250</td><td>mA</td></iout2<2a<>			250	mA
Load Regulation 3	△V03LOAD	-20mA<1 _{OUT3} <-5mA			100	mA
Load Regulation 4	△V04LOAD	$-40 \text{mA} < I_{OUT4} < -10 \text{mA}$			100	mA
Load Regulation 5	AV05LOAD	20mA <itne<40ma< td=""><td></td><td></td><td>200</td><td>mA</td></itne<40ma<>			200	mA
Line Regulation 1	△V01LINE	20mA <i<sub>IN5<40mA 33V<v<sub>IN1<45V</v<sub></i<sub>			250	mA
Line Regulation 2	△V02LINE	7.5V <vin2<20v< td=""><td></td><td></td><td>100</td><td>mA</td></vin2<20v<>			100	mA
Line Regulation 3	△V03LINE	33V <vin1 45v<="" td=""><td></td><td></td><td>100</td><td>mA</td></vin1>			100	mA
Line Regulation 4	^{△V} 04LINE	6.5V <vin5<8v< td=""><td></td><td></td><td>100</td><td>mA</td></vin5<8v<>			100	mA
Quiescent Current 1	LCC1	TN2		6.5	9.0	mA
Quiescent Current 2	ICC2			-	12.0	mA
Input-Output Voltage Drop	v_{D1}^{UU2}	$V_{OUT1} \Delta V_{01} = 10\%$,			1.3	V
	וע	$I_{OUT1}=35mA$			1•5	•
	V _{D2-1}	V _{OUT2} △V _{O2} =10%, I _{OUT2} :	=1A		1.4	v
	v _{D2-2}	V _{OUT2} △V _{O2} =10%,I _{OUT2}	=2A		1.9	v
Saturation Voltage at	V ₀₂ OFF(sat)	$I_{OUT2} = -1A$			1.4	v
V _{OUT2} OFF Mode	U2 UFF(Sat)	-0012			1.47	v

Pin Assignment



Pin No.	Pin Name	Pin No.	Pin Name
1	V OUT 1	6	V IN2
2	V IN1	7	Vουτ2
3	V ουτ5	8	GND
4	V OUT4	9	R
5	MT	10	Vоитз

Block Diagram and Sample Application Circuit



No.1595-2/3

į

- No products described or contained herein are intended for use in surgical implants, life-support systems, aerospace equipment nuclear newer control systems, vehicles, disaster/orime-traventice, equipment and
- aerospace equipment, nuclear power control systems, vehicles, disaster/crime-prevention equipment and the like, the failure of which may directly or indirectly cause injury, death or property loss.
- Anyone purchasing any products described or contained herein for an above-mentioned use shall: ① Accept full responsibility and indemnify and defend SANYO ELECTRIC CO., LTD., its affiliates, subsidiaries and distributors and all their officers and employees, jointly and severally, against any and all claims and litigation and all damages, cost and expenses associated with such use:
 - Not impose any responsibility for any fault or negligence which may be cited in any such claim or litigation on SANYO ELECTRIC CO., LTD., its affiliates, subsidiaries and distributors or any of their officers and employees jointly or severally.
- Information (including circuit diagrams and circuit parameters) herein is for example only; it is not guaranteed for volume production. SANYO believes information herein is accurate and reliable, but no guarantees are made or implied regarding its use or any infringements of intellectual property rights or other rights of third parties.